



**Course Outcomes**



- Ability to solve electrical circuits with Graphs.
- To learn techniques of solving circuits involving different active and passive elements.
- To analyze the behaviors of the circuit's response in time domain.
- To analyze behavior of the circuit's response in frequency domain.
- To understand the significance of network function.

**Model Question Paper**

**Course: Networks**

**Analysis and Synthesis**

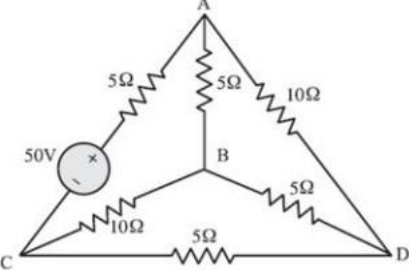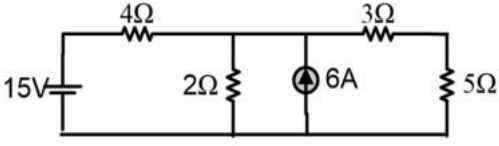Q.No	Question	Marks	CO	BL	PI Code
1a	Obtain the oriented from the given Cut-set matrix: $[Q] = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \end{bmatrix}$	8	1	L3	1.4.1
1b	Find out the number of possible trees for the figure given below: 	10	1	L2	1.4.1
2a	Define the following terms, (I) Link (II) Graph (III) Tree (IV) Node (V) Branch	8	1	L2	1.4.1
2b	Determine the current flowing through 5 ohms resistance in the network shown below (fig-1) using Thevenin's theorem. 	10	2	L3	3.1.6
3a	Explain about properties of Exponential Response of RLC circuits. Deduce the transient response source free series RL circuit	08	3	L3	2.1.3

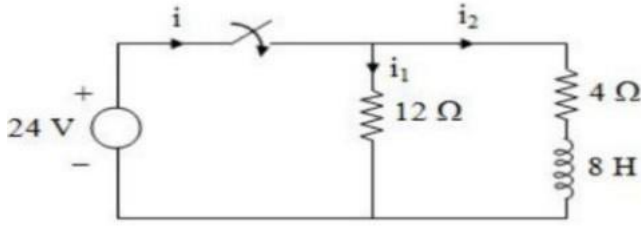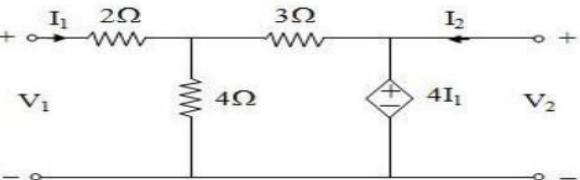Q.No	Question	Marks	CO	BL	PI Code
3b	Find the current $i_2$ for $t > 0$ in the circuit shown below as shown in fig. 	10	3	L2	1.4.1
4a	Derive the condition for maximum power transfer for an ac circuits and applications of maximum power transfer.	8	3	L2	1.4.1
4b	The impedances of parallel circuit are $Z_1 = (4 + j6)$ ohms and $Z_2 = (12 - j8)$ ohms. If the applied voltage is 220V, find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram	10	3	L3	2.1.3
5a	A resistor of $150\Omega$ , inductance of $200\text{mH}$ and a capacitance of $10\mu\text{F}$ are connected in series across $500\text{V}$ , $150\text{Hz}$ supply. Determine the following (i) Impedance (ii) current flowing through the circuit (iii) power factor (iv) voltage across R,L & C (v) power in watts.	10	3	L3	3.1.6
5b	Find Y and Z parameters of the networks as shown in fig 	10	4	L2	1.4.1
6a	The transfer function of a system is $G(s) = \frac{2}{(s+1)(s+2)}$ . Obtain a state variable representation for the system.	10	4	L2	1.4.1
6b	Derive the condition of symmetry for a two-port network and find condition of symmetry in terms of Y parameter.	10	4	L3	3.1.6
7a	A parallel RLC circuit is supplied with a voltage source of $230\text{V}$ , $50\text{Hz}$ . Determine circuit current and power factor if $R=40\Omega$ , $L=0.2\text{H}$ and $C=50\mu\text{F}$ .	08	3	L2	1.4.1
7b	Derive the condition for maximum power transfer for an ac circuits and applications of maximum power transfer.	08	2	L3	3.1.6
8a	Differentiate between Foster and Cauer forms and also write down the steps to obtain Foster-I and Foster-II forms.	08	5	L2	1.4.1

Q.No	Question	Marks	CO	BL	PI Code
8b	How the function can be identified as a positive real function? Explain with a suitable example.	10	5	L3	3.1.6