

Sub Code: VDT-307

ROLL NO.

Model Question Paper

COURSE: M.TECH

BRANCH: VLSI DESIGN

SEMESTER: 1

SUBJECT: Mixed Signal IC Design

Duration: 3:00 hrs

Max marks: 100

Note: - Attempt all questions: All Questions carry equal marks

Q 1. Attempt any four parts of the following (5x4=20)

- Why CMOS Technologies is preferred over other fabrication technologies for Analog-Mix-Signal Integrated Circuits?
- Justify the need of analog circuit components in the era of Digital Transformation.
- Give a comparative analysis of analog continuous time filters and digital filters.
- Explain how a MOSFET can be used as a Current Controlled Current Source.
- Discuss analog design octagon and its significance in analog mixed signal integrated circuits.
- How Z-transform is related to the Laplace transform?

Q 2. Attempt any four parts of the following (10x4=20)

- What is switched capacitor? Design a switched capacitor realization for a first order, high pass circuit with a high frequency gain of -10 and a -3dB frequency of 1 kHz using a clock of 100kHz
- Draw the circuit diagram and explain the working of a Switched Capacitor (SC) integrator.
- Discuss key technical challenges and market challenges before mixed signal IC design engineers and also discuss some important manufacturers leading the market in the field of Mixed signal ICs.

Q 3. Attempt any two parts of the following (10x2=20)

- With neat diagram, explain the working of a sample and hold circuit.
- Give the classification of ADC architectures based on the conversion rate. Also explain the static and dynamic characteristics of ADCs.
- What is time interleaving? Explain the operation of a time interleaved ADC.

Q4. Attempt any two parts of the following: (10x2=20)

- What are the dynamic characteristics that influence the performance of DACs?
- What is a flash converter? Discuss the working of a 3-bit flash A/D Converter.
- Write short critical note on hybrid data converters.

Q5. Attempt any two parts of the following: (10x2=20)

- Explain the dynamics of a simple PLL Circuit. Also explain the Jitter in PLLs and delay locked loops.
- Draw the block diagram of a charge pump PLL and explain the functions of each block.
- Differentiate the working of analog PLL circuits from digital PLL Circuits. With the help of necessary waveforms, explain about the non-ideal effects in PLLs.